

TEST CASE 1

```
Scilab 2025.1.0 Console
frequency = 100.000000 MHz
length of lambda/4 transformer = 3.000000 meters
characteristic impedance of quarter wave line = 70.710600 ohms

frequency = 200.000000 MHz
length of lambda/4 transformer = 1.500000 meters
characteristic impedance of quarter wave line = 70.710600 ohms

frequency = 300.000000 MHz
length of lambda/4 transformer = 1.000000 meters
characteristic impedance of quarter wave line = 70.710600 ohms

frequency = 500.000000 MHz
length of lambda/4 transformer = 0.600000 meters
characteristic impedance of quarter wave line = 70.710600 ohms

-->
```

TESTCASE 2

```
Scilab 2025.1.0 Console
Input impedance = 25.000000 ohms
Load impedance = 100.000000 ohms
length of lambda/4 transformer = 0.150000 meters
characteristic impedance of quarter wave line = 50.000000 ohms
-----
Input impedance = 50.000000 ohms
Load impedance = 100.000000 ohms
length of lambda/4 transformer = 0.150000 meters
characteristic impedance of quarter wave line = 70.710600 ohms
-----
Input impedance = 75.000000 ohms
Load impedance = 100.000000 ohms
length of lambda/4 transformer = 0.150000 meters
characteristic impedance of quarter wave line = 86.602500 ohms
-----
Input impedance = 100.000000 ohms
Load impedance = 100.000000 ohms
length of lambda/4 transformer = 0.150000 meters
characteristic impedance of quarter wave line = 100.000000 ohms
-----
--> |
```